




ELEC1100: Introduction to Electro-Robot Design

Lecture 7: Transistor and Diode Circuits



ELEC1100 ROADMAP

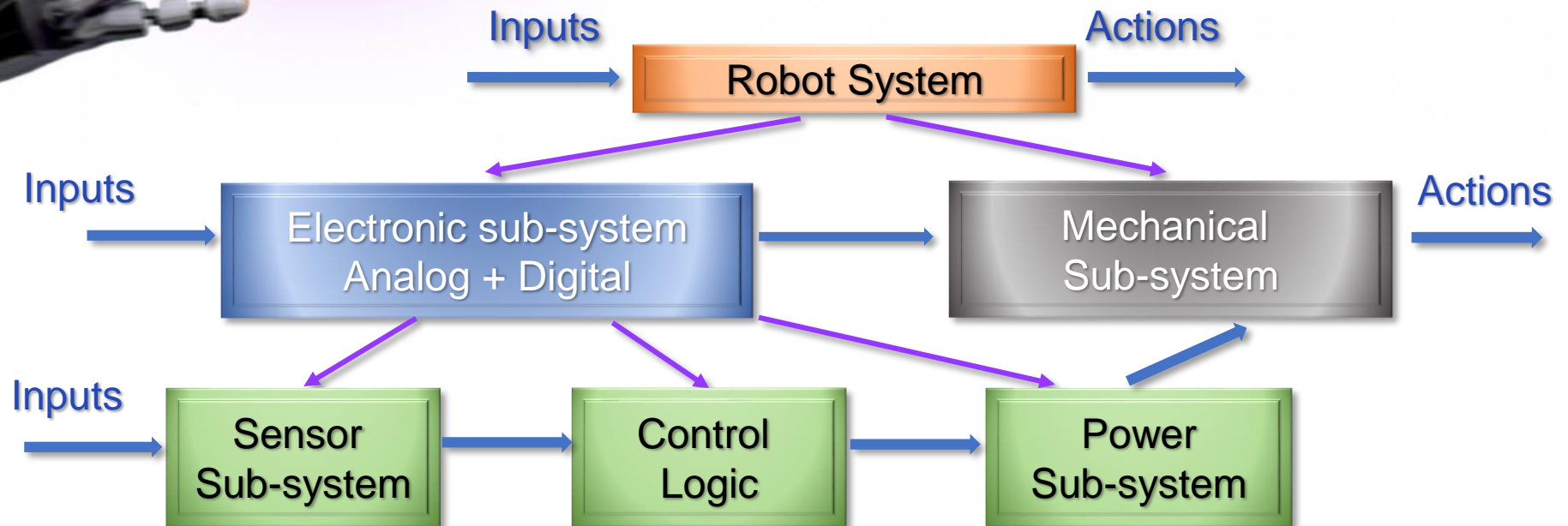

Basic electronics:

- Wk1: Basic Electronics - Charge/Current/Voltage/Resistor
- Wk2: Energy/Power and DC Sources

Motor Power Supply:

- Wk3: Pulse Signal and PWM Control
- Wk4: Transistor and H-Bridge





LAST LECTURE


- ❖ A comparator compares 2 binary numbers

$A (=A_3A_2A_1A_0)$ and $B (=B_3B_2B_1B_0)$

- ❖ If $A < B$, the pin $A < B$ will go high and so on

- ❖ Suppose the number A comes from the counter **74HC161** and starting from 0000

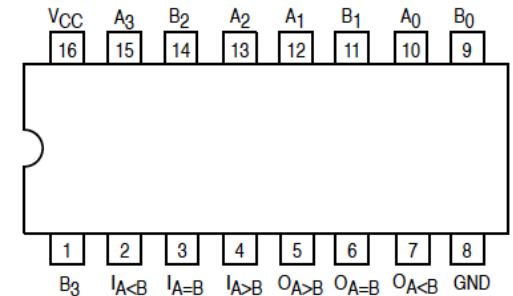- ❖ By inputting a fixed number to B , we can control the duty cycle at output of $A < B$




$O_{A < B}$ output


$B=0$




$B=4$

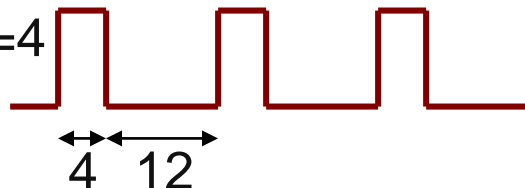

$B=15$

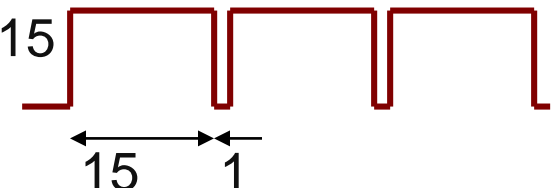


LAST LECTURE

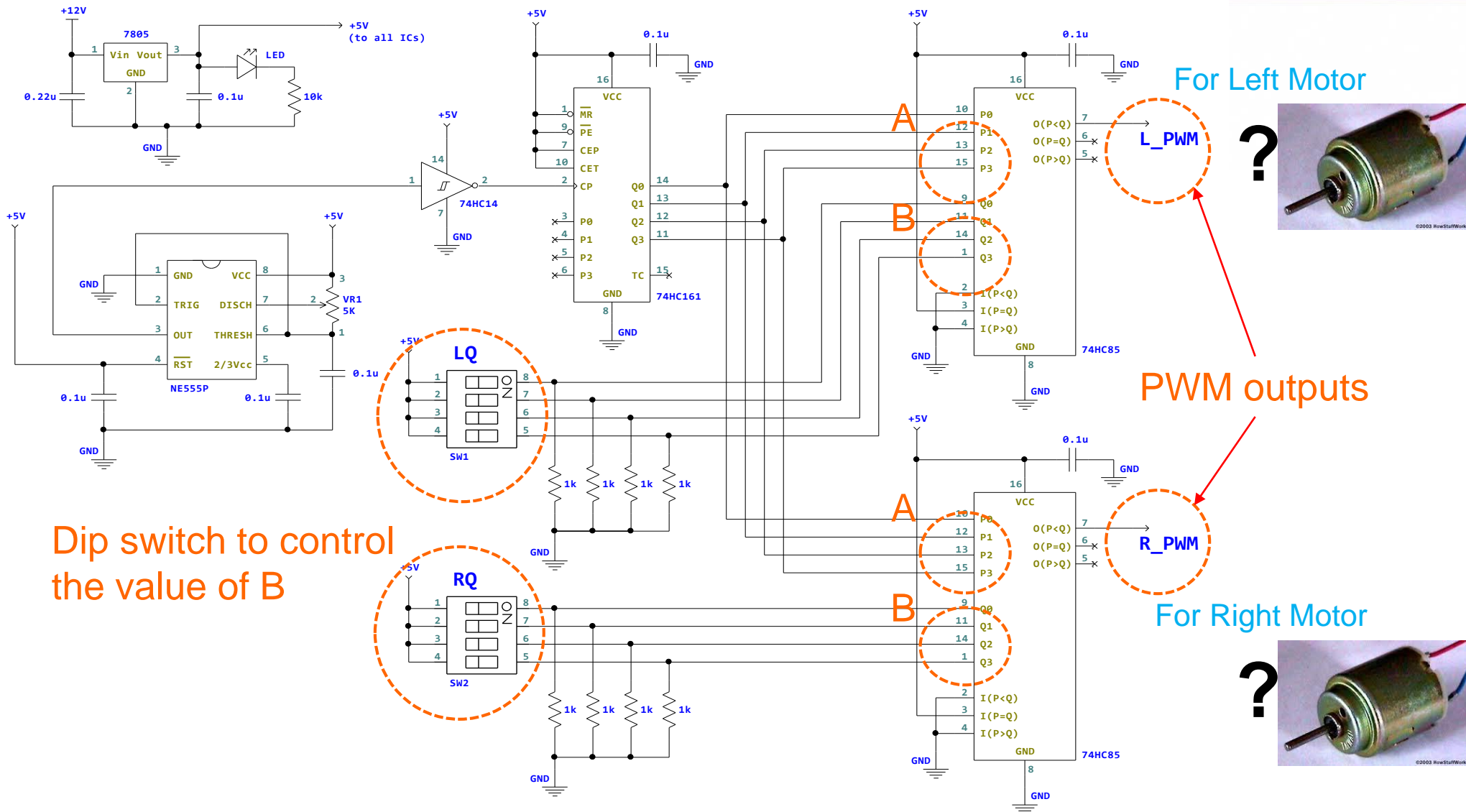



INTERFACING PWM CIRCUIT TO THE MOTOR

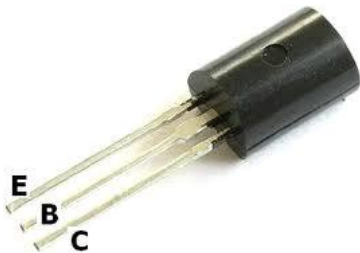- ❖ Brushed motors usually require very high current to drive it. Thus, the driving signal needs to be amplified by a transistor
- ❖ A transistor is a 3-terminal device that can be viewed as a electronic switch
- ❖ The conductivity between two of the terminals is controlled by the third terminal



Transistor



Transistor



analogy



A SHORT HISTORY OF TRANSISTOR

- ❖ Invented in Bell Labs by William Shockley, John Bardeen and Walter H. Brattain




- Shockley: “one of the century’s most important scientists”, Times Magazine
- Bardeen: won Nobel Prize twice !
- The three of them won the 1956 Nobel Prize in Physics for inventing the transistor

- ❖ Bardeen and Brattain made the breakthrough and Shockley put a nice ending
- ❖ However Shockley was not a good leader. Brattain refused to work for him anymore and Bardeen just quit



THE SILICON VALLEY

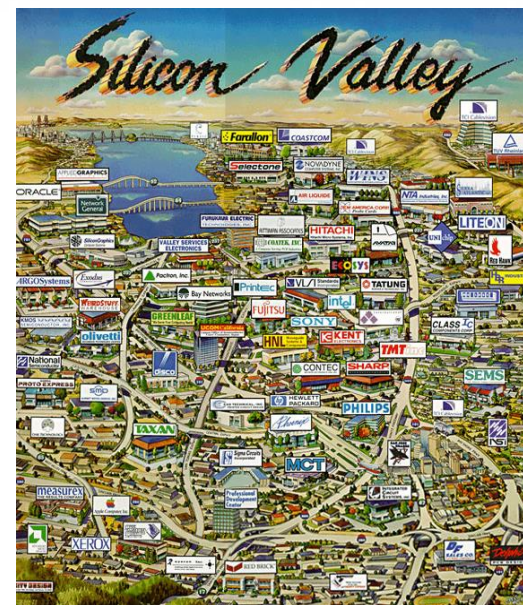- ❖ Shockley moved to Stanford and founded Shockley Semiconductors in Palo Alto, the beginning of Silicon Valley





- ❖ Shockley hired the brightest scientists and engineers (e.g. Gordon Moore and Bob Noyce, founders of Intel) who founded many companies after they left Shockley





THE FIRST TRANSISTOR

- ❖ Resemble the schematic shown earlier

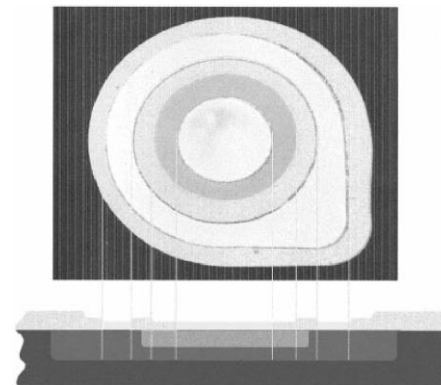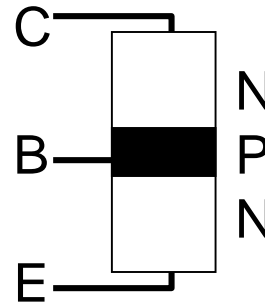



Modern planar
transistors








BIPOLAR JUNCTION TRANSISTOR (BJT)

- ❖ There are two types of standard BJT

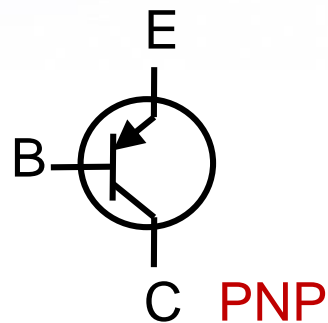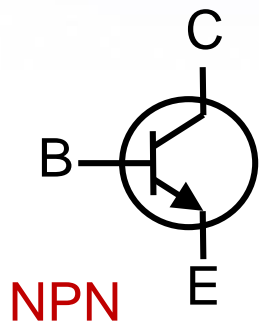



or

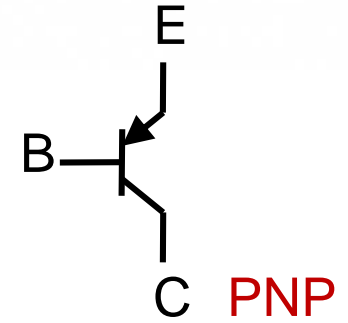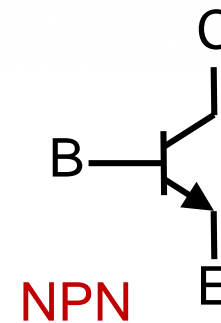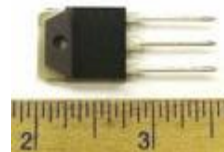

- ❖ The leads are labeled Collector (**C**), Base (**B**) and Emitter (**E**)

➤ The N and P refers to the material type that is used to construct the transistor

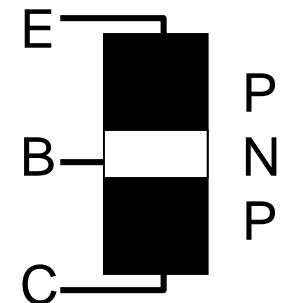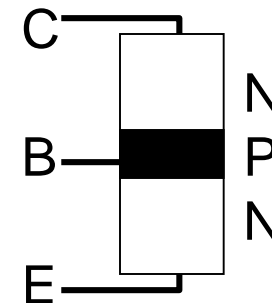
- ❖ Detail operation will be covered in other courses






TRANSISTORS AS SWITCHES

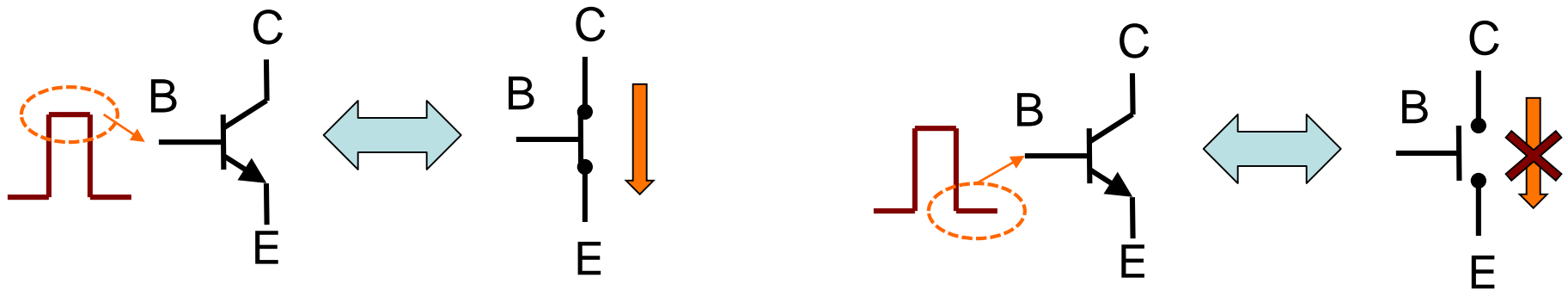❖ Simple equivalent of **NPN** transistors



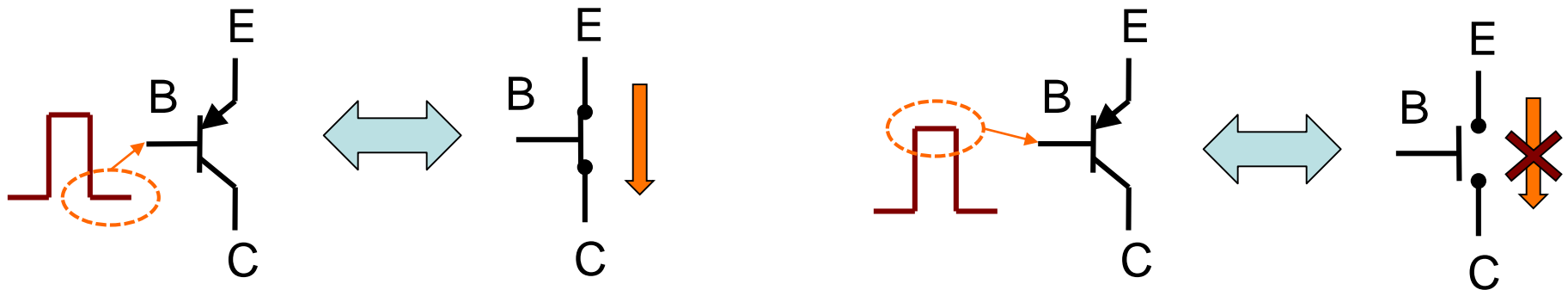
❖ Simple equivalent of **PNP** transistors





MORE REALISTIC OPERATION OF A BJT

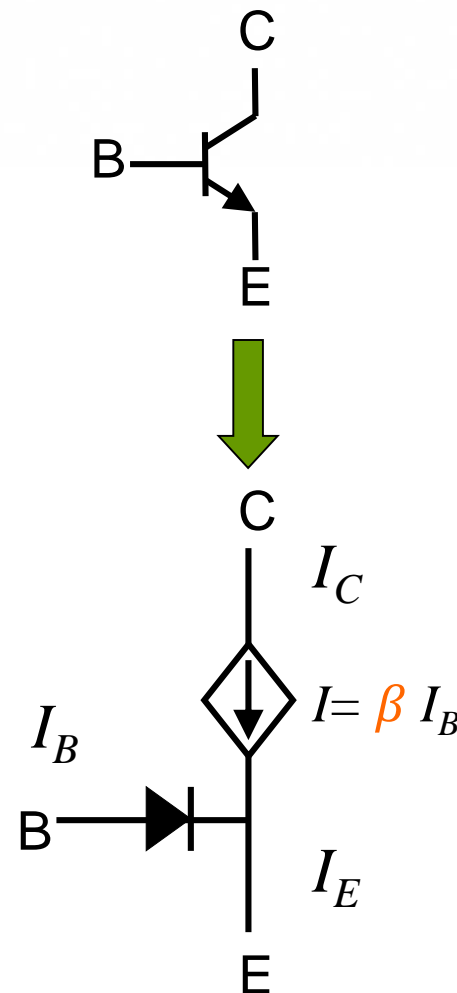- ❖ The B-E terminal of a BJT is actually behaving like a diode
- ❖ A base current I_B flows only when the voltage V_{BE} across the base-emitter junction is about $0.7V$
- ❖ Collector current is proportional to the base current, i.e., $I_C = \beta I_B$ where β is the current gain.
- ❖ β is in the range of 20-200, leading to an amplification of current






-
- Diagram illustrating the simplification of a diode's I-V characteristic curve.
- real I-V curve**
- On region: $I = I_0 \left(e^{\frac{qV}{kT}} - 1 \right)$
- Off region: $V < V_{on}$
- simplify**
- Ideal I-V curve**
- On region: $V > V_{on} = 0.7V$
- Off region: $V < 0.7V$
- Diode symbol: V
- Simplified circuit: $0.7V$
- when $V > 0.7V$
- when $V < 0.7V$



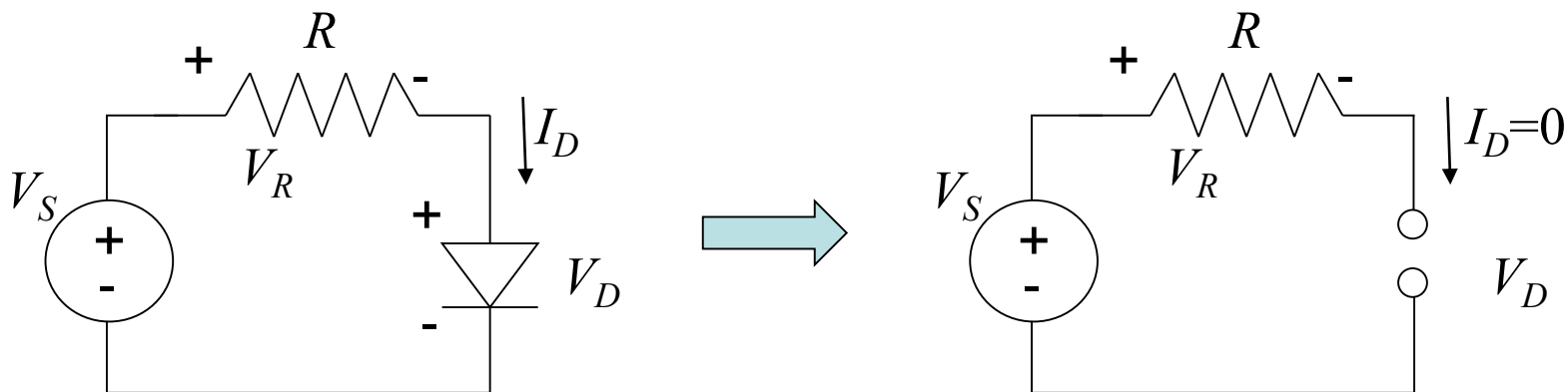EXAMPLE OF DIODE CIRCUITS

- ❖ Assume off region, replace it with the equivalent model




$$I_D = 0 \Rightarrow V_R = 0 \Rightarrow \boxed{V_D = V_S}$$

- ❖ If $V_S < 0.7V$, the assumption is correct and answer found
- ❖ Otherwise, assumption is wrong and we try the other case




CURRENT THROUGH THE DIODE

❖ When $V_S > 0.7V$


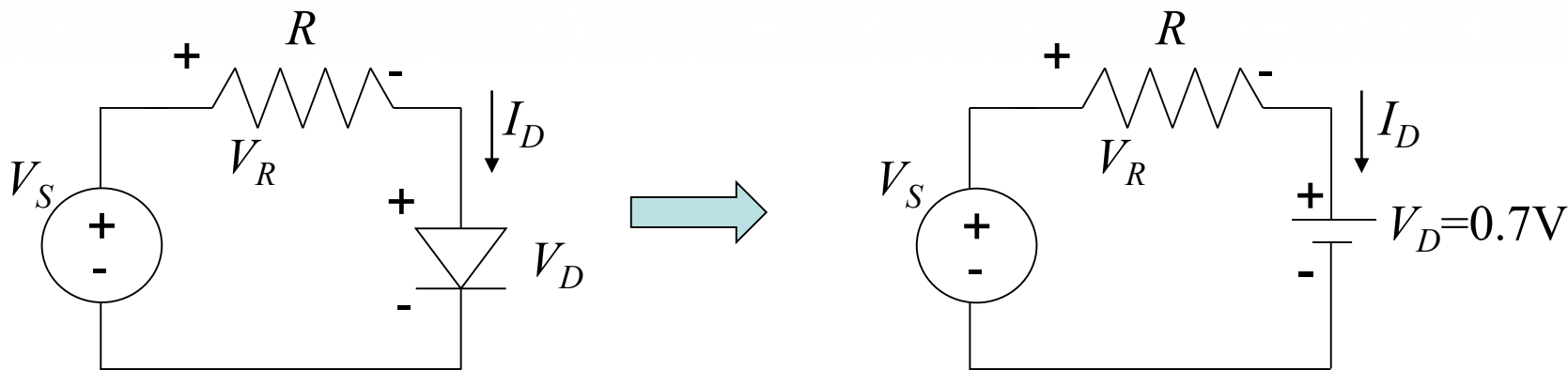


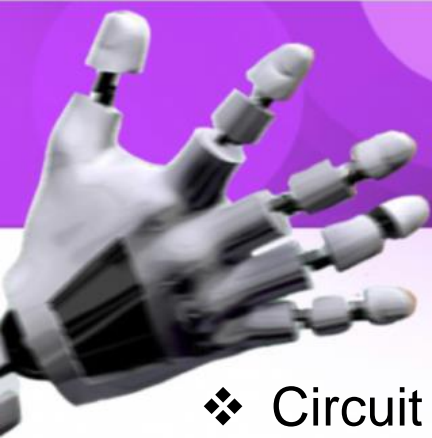- ❖ We can obtain $V_S - 0.7 = V_R \Rightarrow I_D = \frac{V_S - 0.7}{R}$
- ❖ If the condition is incorrect (or $V_S < 0.7V$), $I_D < 0$
- ❖ It is important to have a resistance in series with a diode, or the current can be very large



CIRCUIT WITH TWO DIODES

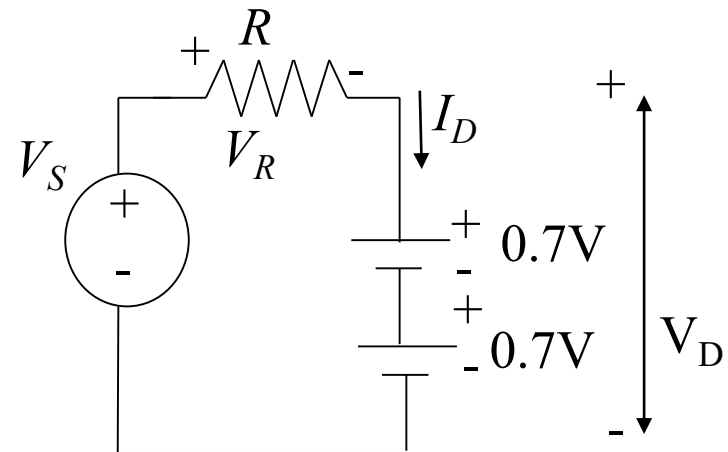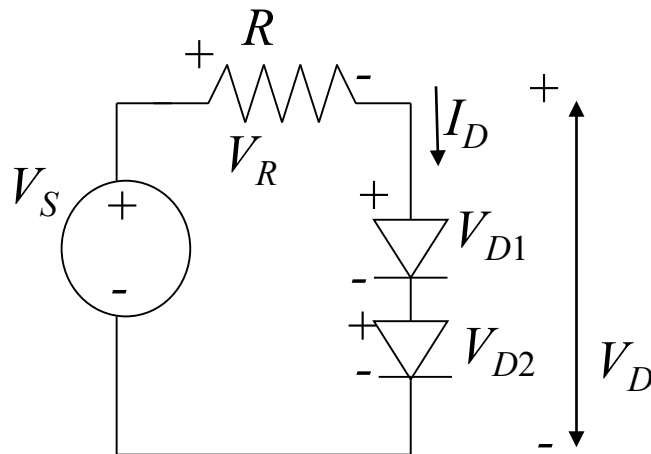- ❖ Circuit with two diodes can be solved in the same approach



- ❖ It is simple and leave it to you as an exercise




BACK TO TRANSISTOR

- ❖ A resistor is always needed at the base to avoid a very high current

$$I_B = \frac{V_{IN} - 0.7}{R_B}$$

- $I_B = 0$, transistor is off
- I_B small: active mode with transistor partially on
- I_B large: transistor fully on

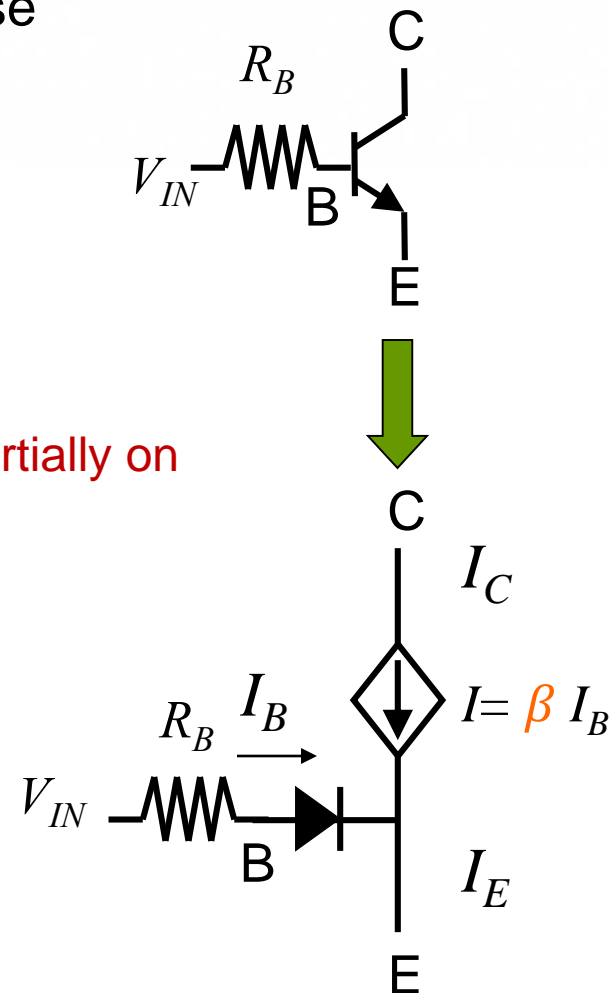
- ❖ As long as the input voltage V_{IN} is larger than $0.7V$, you can consider the transistor is on (either partially or fully)





CIRCUIT EXAMPLE: LIGHT ACTIVATED SWITCH

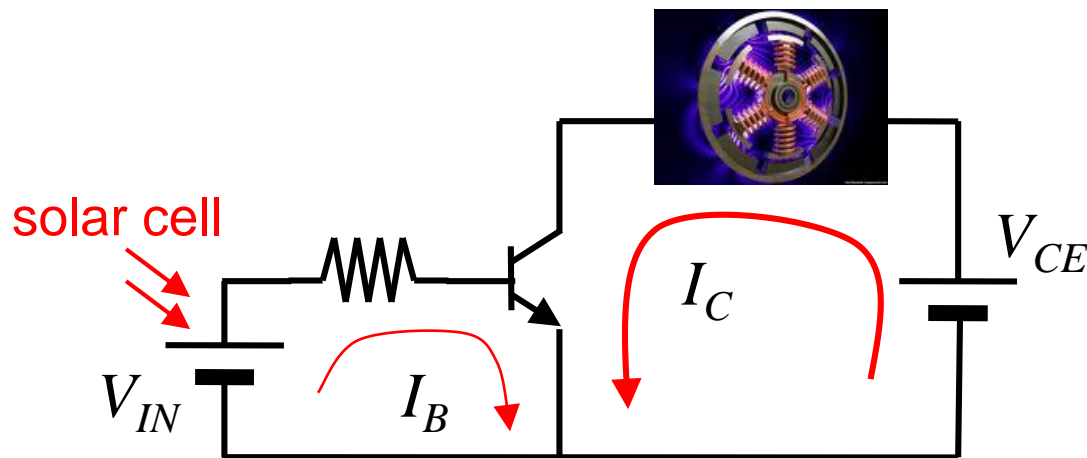- ❖ Consider a circuit to turn on a fan under strong light
- ❖ You may simply connect the fan to a solar cell, but the solar cell is not powerful enough to drive the motor
- ❖ Consider using a solar cell to give the V_{BE} of a NPN transistor




- Can use a small power to control the delivery of a large power
- A transistor can be used as an “amplifier”




PNP TRANSISTOR

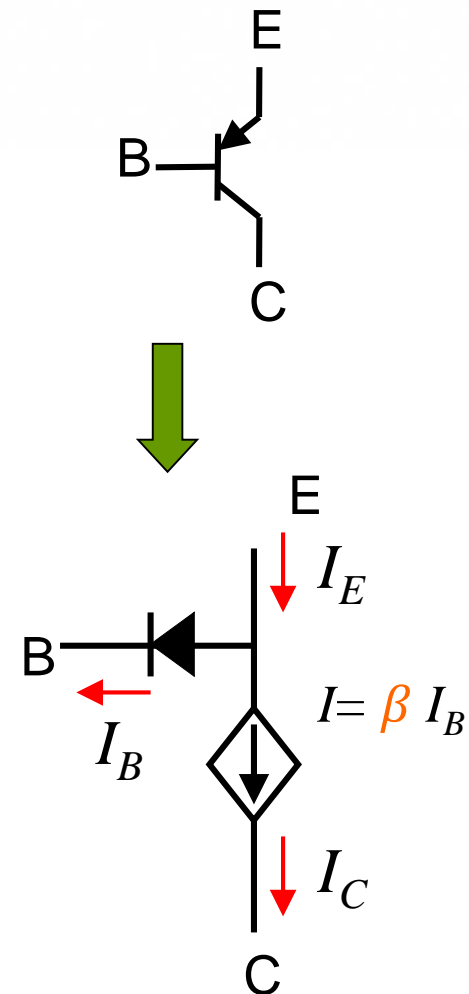- ❖ PNP transistor is similar to NPN, but the diode is between the power supply and the input
- ❖ As long as $V_{BE} < -0.7V$, you may consider the transistor to be on
- ❖ Allow a switch to be turned on with low voltage



CIRCUIT EXAMPLE WITH PNP TRANSISTORS

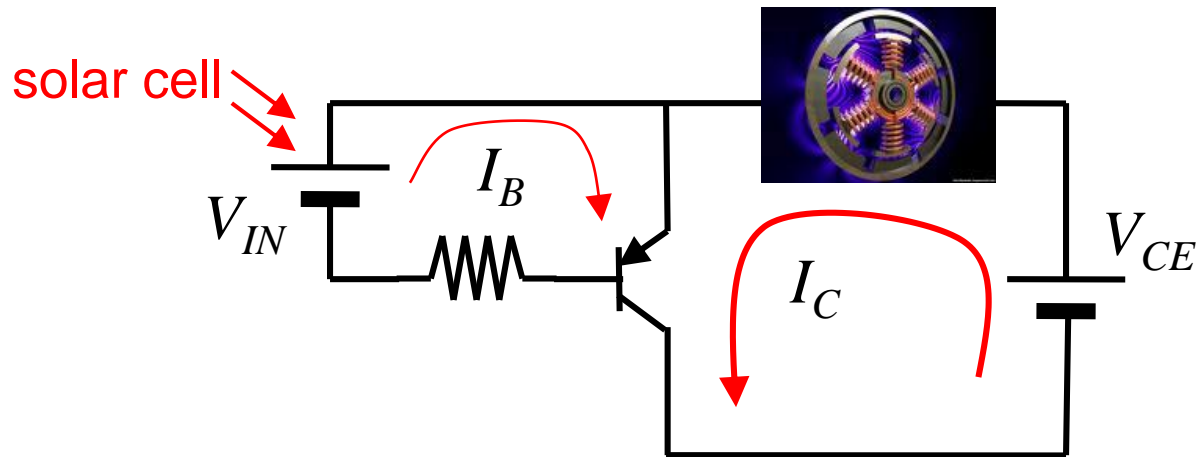- ❖ For the same circuit to turn on a fan under strong light using PNP transistor looks like the following:




- ❖ The performance is exactly the same as the NPN case



LECTURE SUMMARY

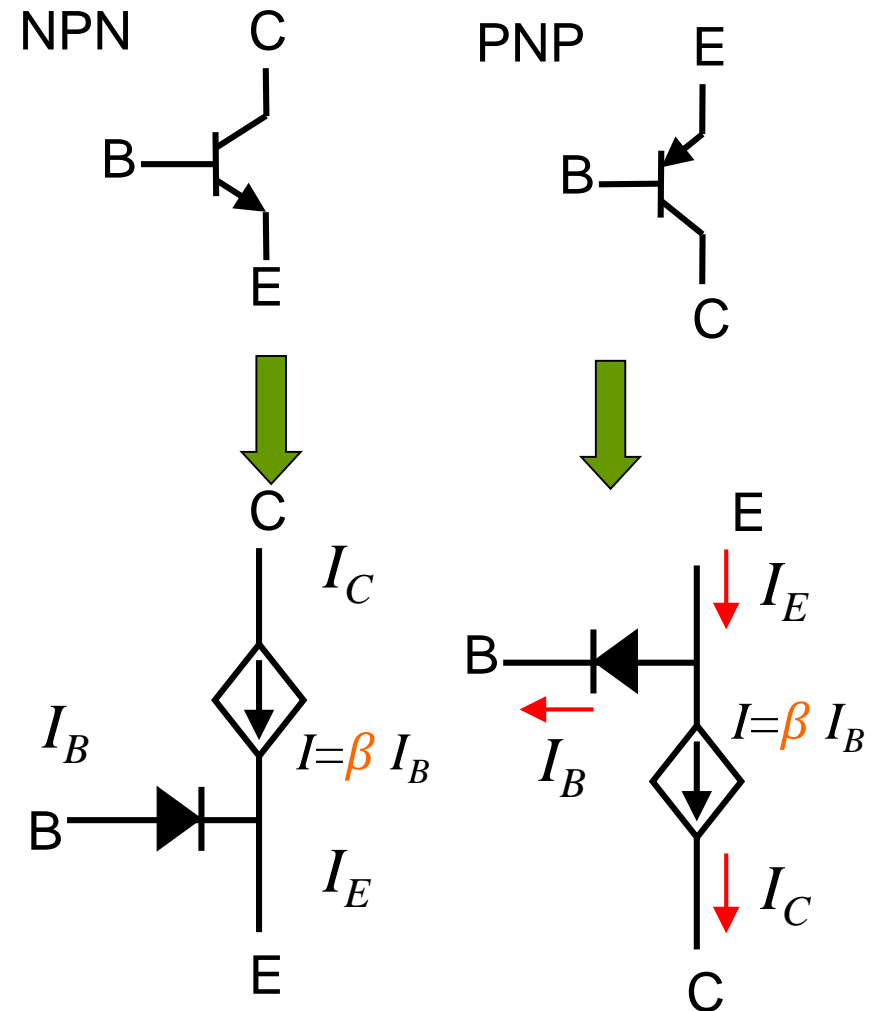- ❖ NPN and PNP transistors and their equivalent circuits
- ❖ Calculating diode current by assuming it is either a battery or an open circuit
- ❖ Transistors can be used as a switch or an amplifier





NEXT LECTURE

- ❖ Transistors as motor control switches
- ❖ H-bridge circuit
- ❖ Transistor as an amplifier



QUESTIONS?

